

BASIC RTL TRAINING PROBLEMS



Guidelines to Solve the problems:-

- 1) Go through the RTL Coding guidelines.
- 2) Use notepad++ extensively to write the RTL files when using windows machines for RTL development whereas on Linux machine it is user choice.
- 3) All RTL code must be in System Verilog and be Synthesizable.

Problem 1: Generate Pulse of Variable Duration

Generate a pulse of programmable duration. Pulse duration and pulse period is compile-time programmable (Use parameter).

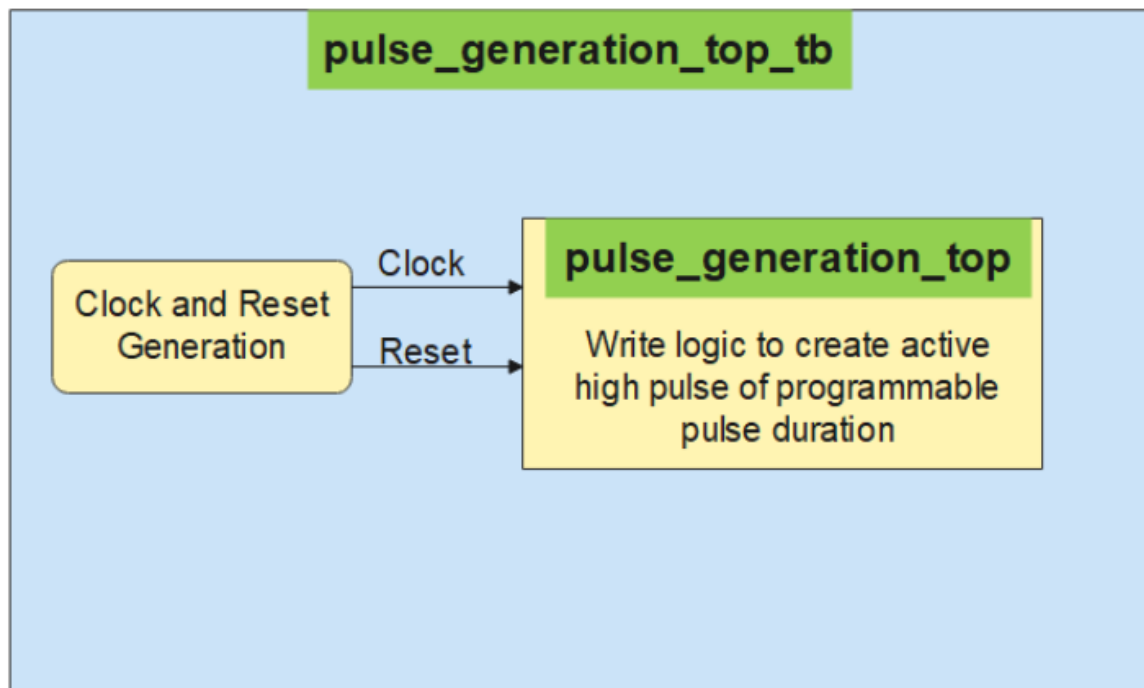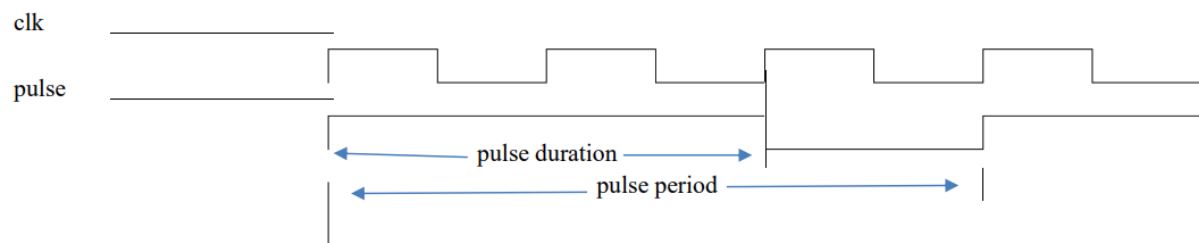- 1) Design Pass Criteria: Pulse duration should be same as expected.
- 2) Try with Different values of pulse duration and pulse period. Pulse duration < pulse period
- 3) If pulse duration > pulse period, then error should be displayed in log.



Eg: - The unit of pulse duration will be 1 clock cycle i.e, if pulse duration is 2 and pulse period is 3 then pulse should be HIGH for 2 clock cycle and LOW for 1 clock cycle.

Problem 2: Logical operation and pipelining

- 1) A, B, C and D are 4 inputs of 8 bit each.
- 2) $E = A \text{ OR } (B \text{ AND } C)$, $F = ((B \text{ AND } C) \text{ XOR } (A \text{ OR } D))$
- 3) Output = 1 whenever E equal to F
- 4) E should be calculated in two clock cycles and F should be calculated in three clock cycles and pipeline should be maintained for correct operation.


A, B, C and D are generated from a 32-bit free running counter where

A= counter [7:0]

B= counter [15:8]

C= counter [23:16]

D= counter [31:24]

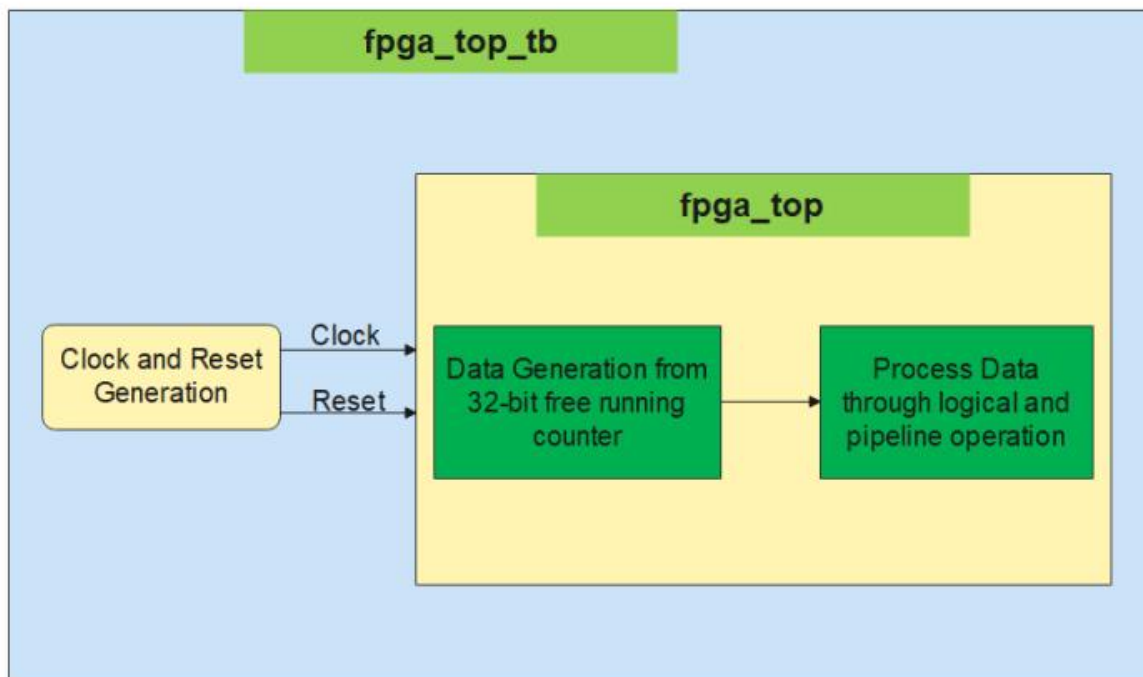

Problem 3: Write a state machine to detect a pattern of “PRESENT MONTH and DATE”.

- 1) Take the present date (LSB 5-bit) and month (MSB 4-bit) as a pattern and convert it into binary number, **For example**, Today is 23rd Nov (23/11), So our Pattern is 11(4'b1011)_23(5'b10111) -> **9'b1011_10111**
- 2) Data generator should generate a 10-bit incremental pattern. This 10-bit parallel data should be converted into serial data.
- 3) The one-bit data is received by detector block. So Incremental data should be updated in every 10 clock cycles.
- 4) Detector block detects the output pulse every time when it detects the required pattern.

